
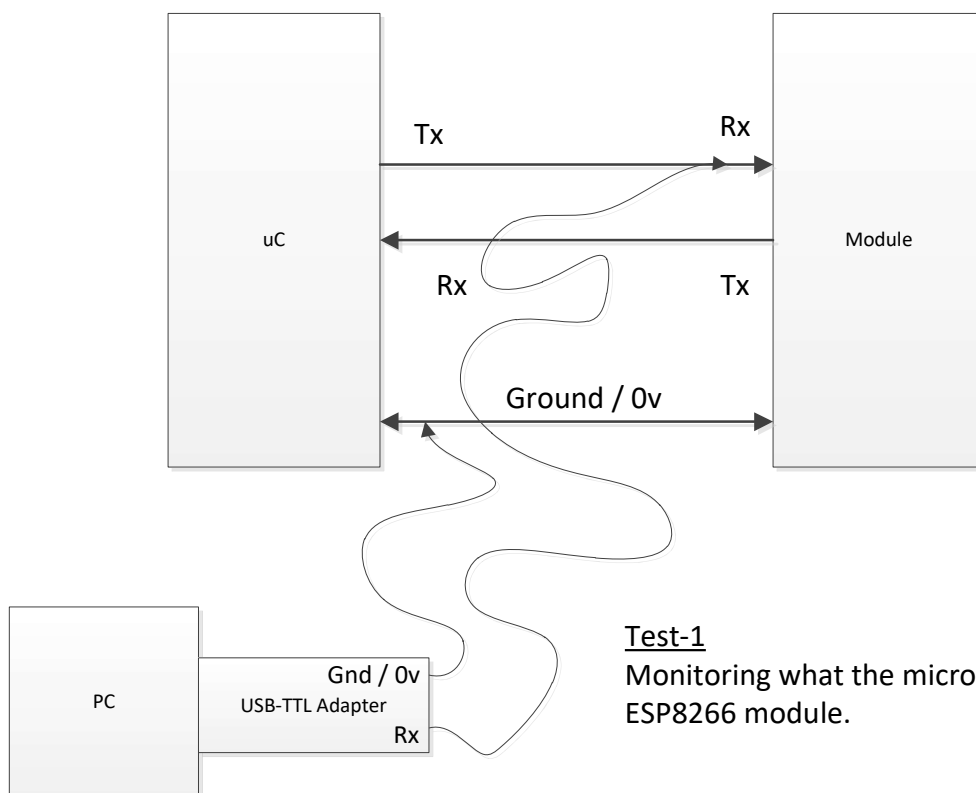


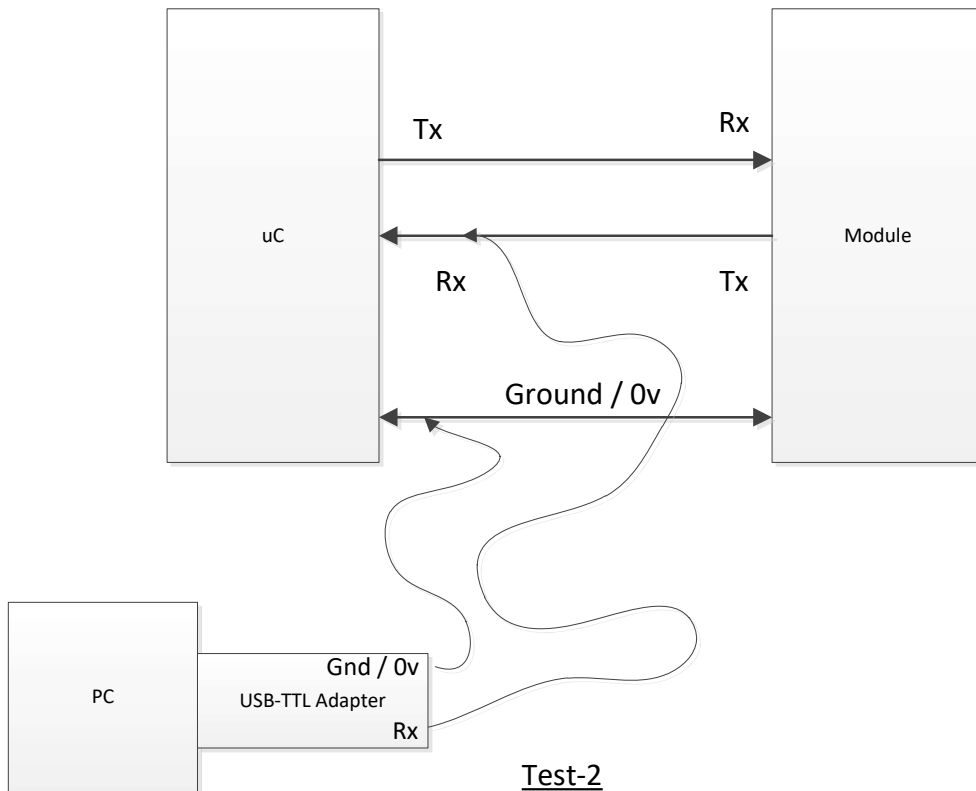General connections between Microcontroller and ESP8266 module. Note you may need a voltage divider between uC Tx and module Rx.




### Test-1

Monitoring what the microcontroller is sending to the ESP8266 module.


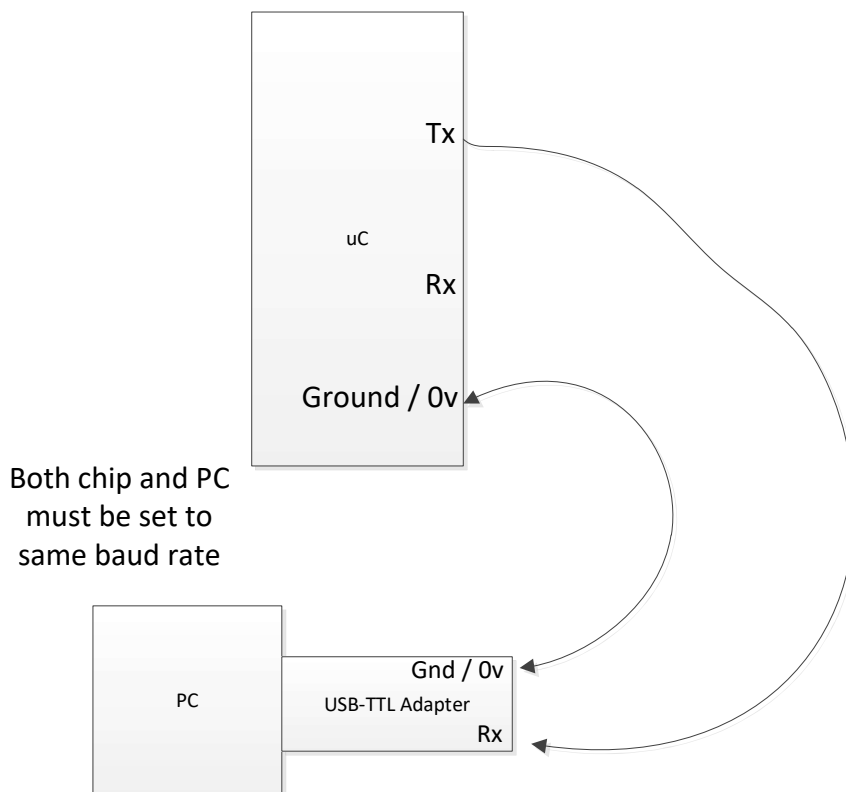
### Test-2

Monitoring what the ESP8266 is sending to the Microcontroller.



Both chip and PC must be set to same baud rate

### Test-3

Monitoring the output of the Microcontroller directly.  
Note you may need a voltage divider.